



Green University

ASSIGNMENT

CLP-04

Section : DC-221

Name : Khondokar Saim

ID : 221902353

Lecturer : Md. Sultanul Islam Ovi

Subject : CSE-204 DC

Date : 08 / 06 / 2023

Task number 01 : Implement the J-K flip-flop and verify with the truth table.


Component List :

Name	Quantity	Component
U1	1	Dual J-K Flip-Flop
FUNC1	1	1 Hz, 5 V, 2.5 V, Square Function Generator
D1 D2	2	Red LED
R1 R2	2	0.2 k Ω Resistor
R3 R4	2	1 k Ω Resistor
P1	1	5 , 5 Power Supply
SW1	1	DIP Switch SPST x 4


Truth Table :

Clk	J	K	Q	Q'	State
1	0	0	Q	Q'	No change in state
1	0	1	0	1	Resets Q to 0
1	1	0	1	0	Sets Q to 1
1	1	1	-	-	Toggles

Tinkercad Circuit View :

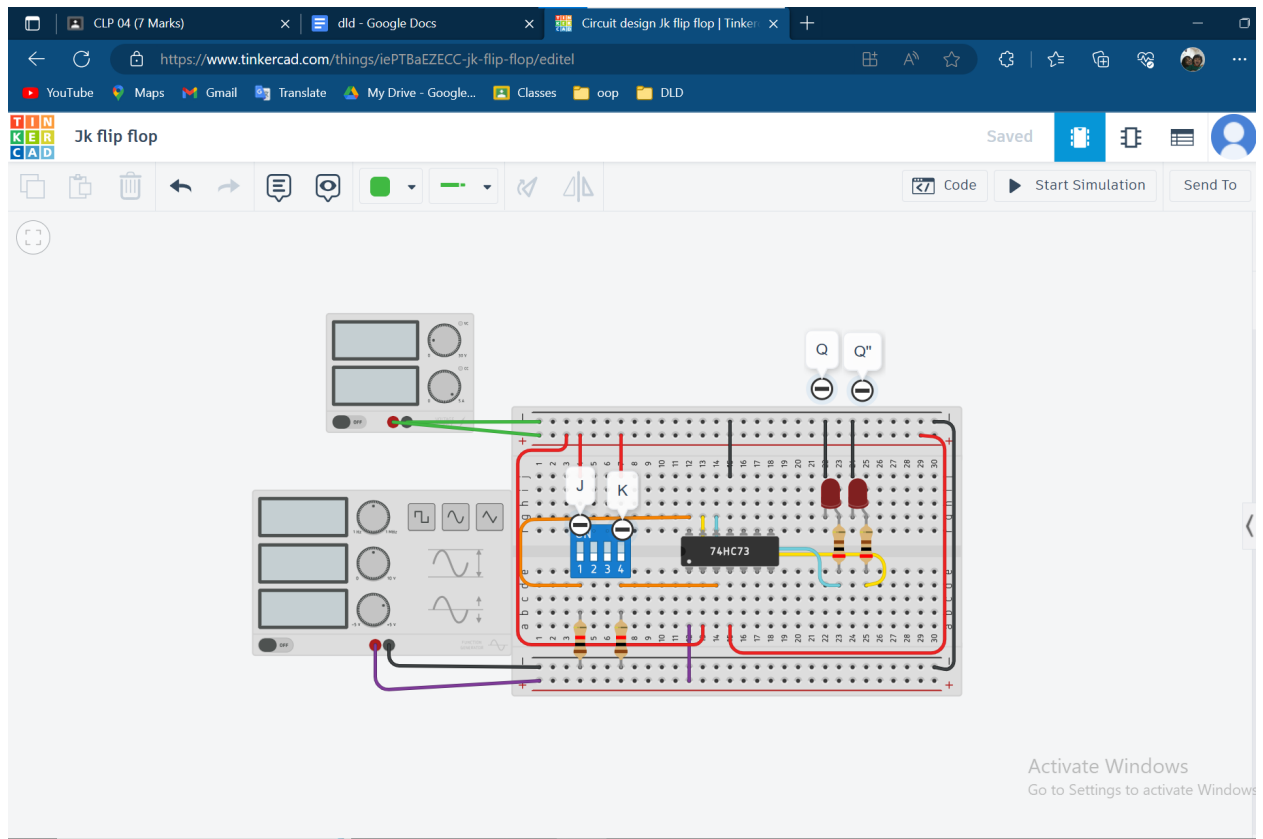


Implementation JK flip flop :

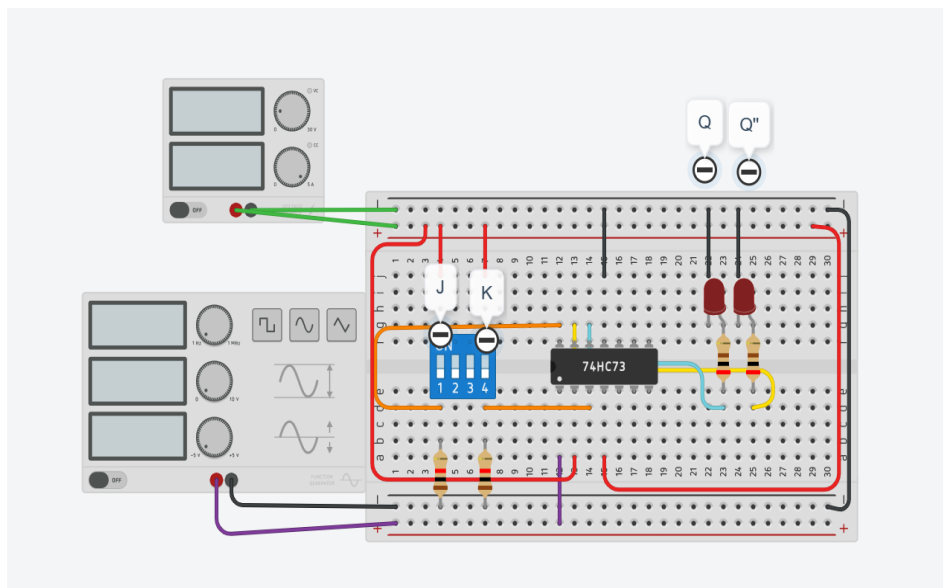

Here

$J = 0$
 $K = 0$
 $Q = Q$
 $Q' = Q'$

STATE =
 NO CHANGE IN
 STATE

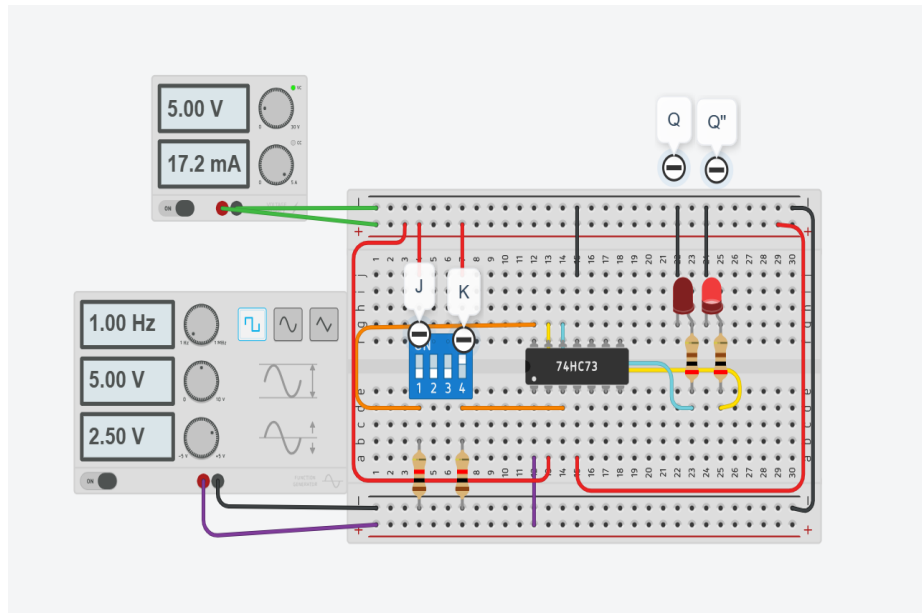

Here

$J = 0$


$K = 1$

$Q = 0$

$Q' = 1$

STATE =

RESET Q TO 0

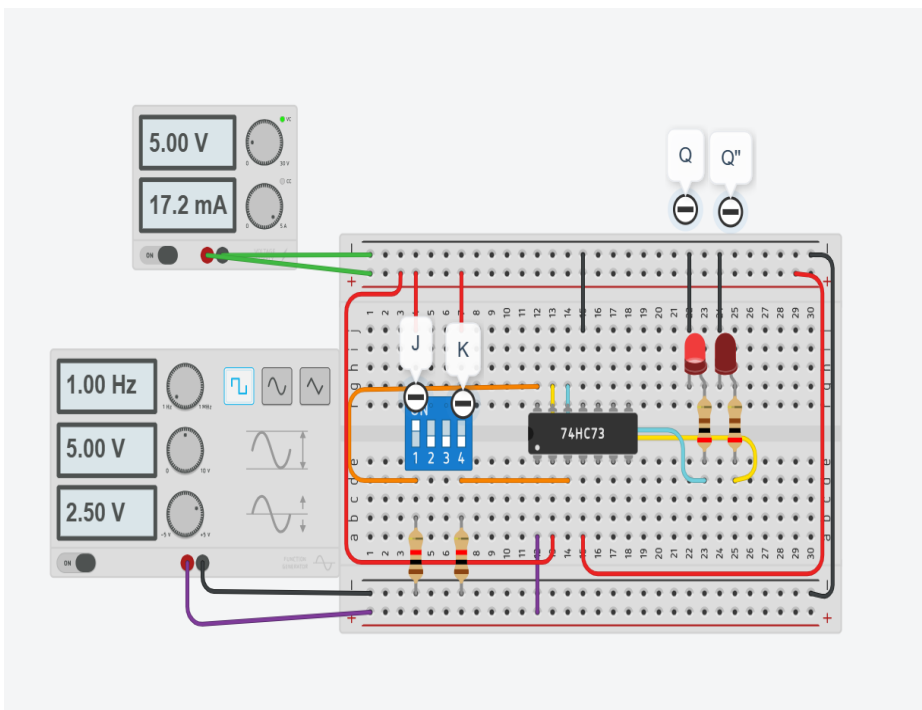

Here

$J = 1$


$K = 0$

$Q = 1$

$Q' = 0$

STATE =

SETS Q TO 1

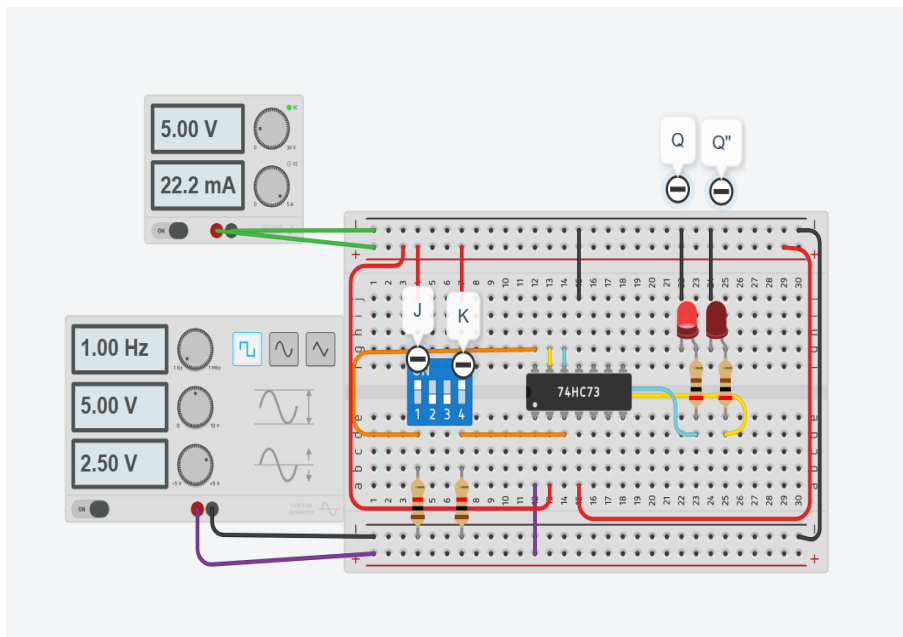

Here

$J = 1$


$K = 1$

$Q = Q''$

$Q'' = Q$

STATE =

TOGGLES

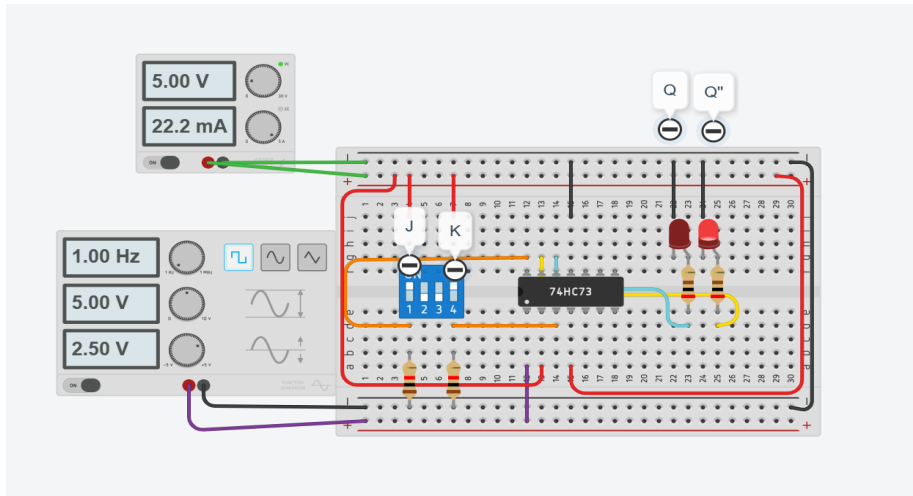


Task number 01 :




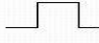
Implement a master slave flip-flop with the J-K flip-flop and verify with the truth table.

Component List :


Name	Quantity	Component
P1	1	5 , 5 Power Supply
U1	1	Hex Inverter
U2	1	Dual J-K Flip-Flop
FUNC1	1	1 Hz, 5 V, 2.5 V, Square Function Generator
U3	1	100 ms Oscilloscope
D1	1	Red LED
R1 R2 R3	3	1 kΩ Resistor
SW1	1	DIP Switch SPST x 4
D2 D3	2	Blue LED

Truth Table :




Truth Table for Master-Slave J-K Flip Flop					
J	K	CLK	Q	Q'	
0	0		Q_0	Q_0'	Hold
0	1		0	1	Reset
1	0		1	0	Set
1	1		Q_0'	Q_0	Toggle (opposite state)

Tinkercad Circuit View :

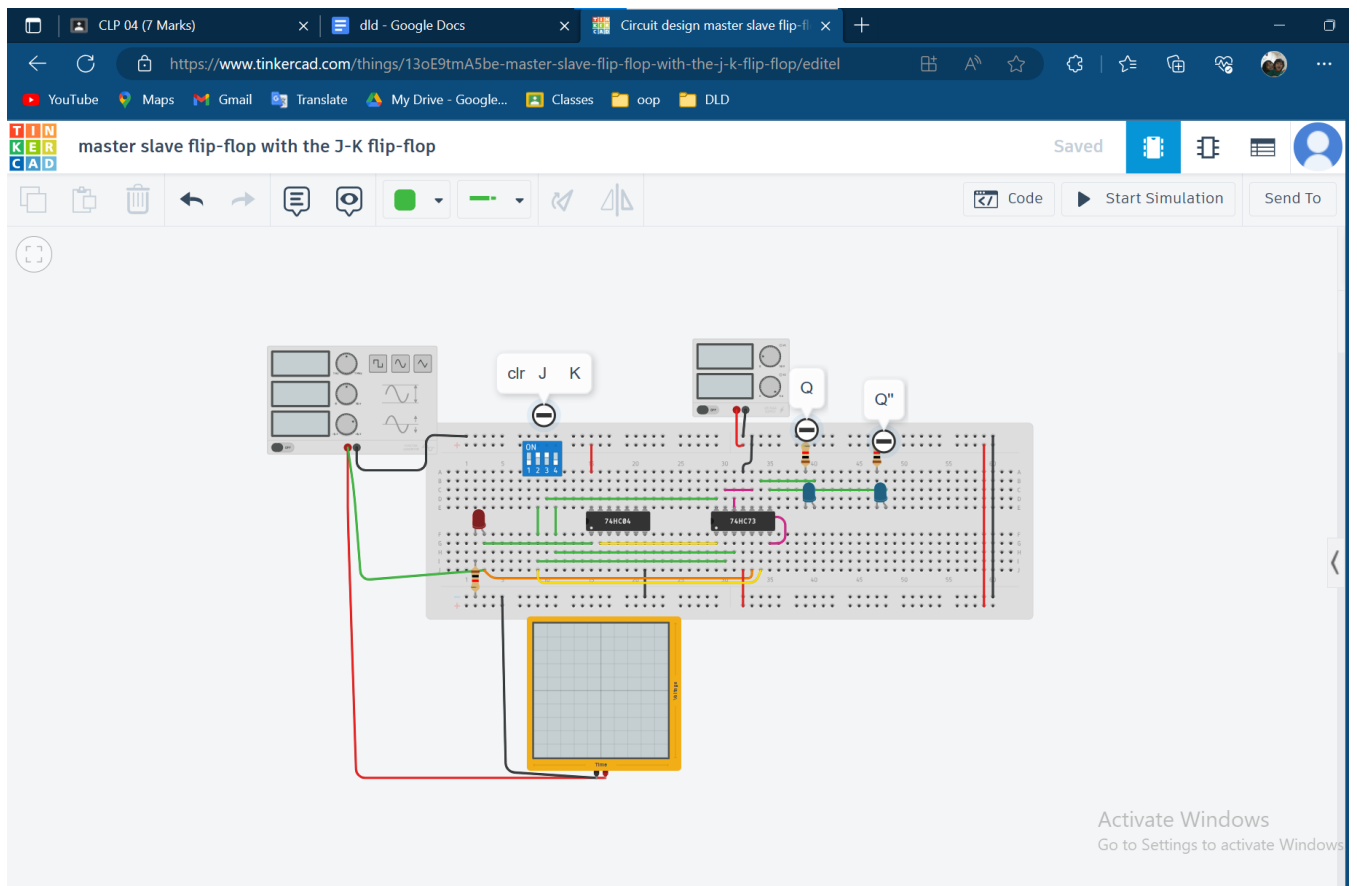

Implementation JK flip flop :

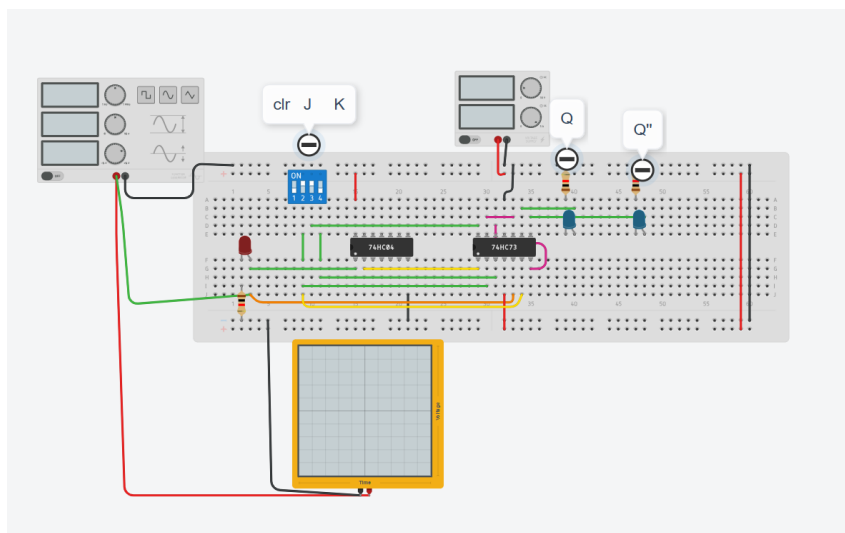

Here

CLK = 1

J = 0



K = 0


Q = Q

Q' = Q'

STATE =

HOLD

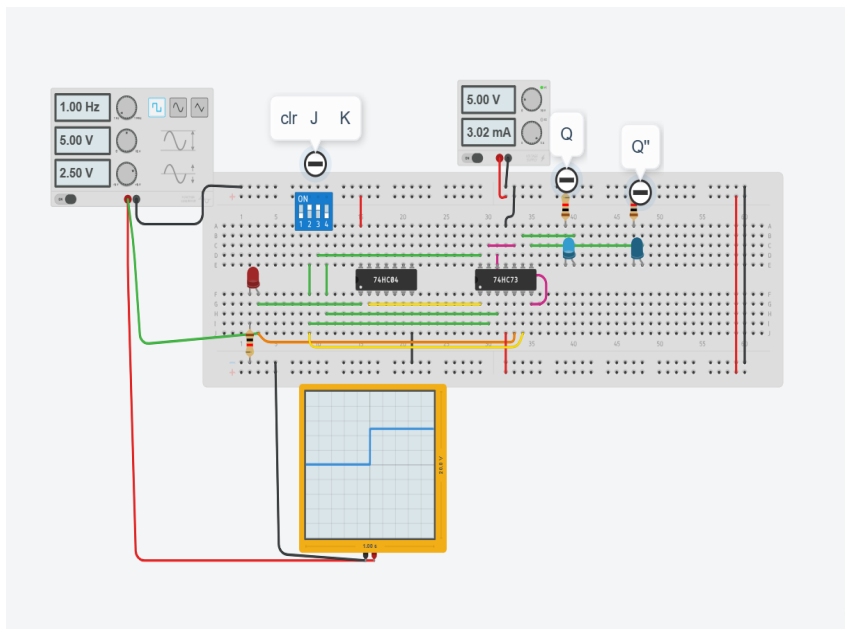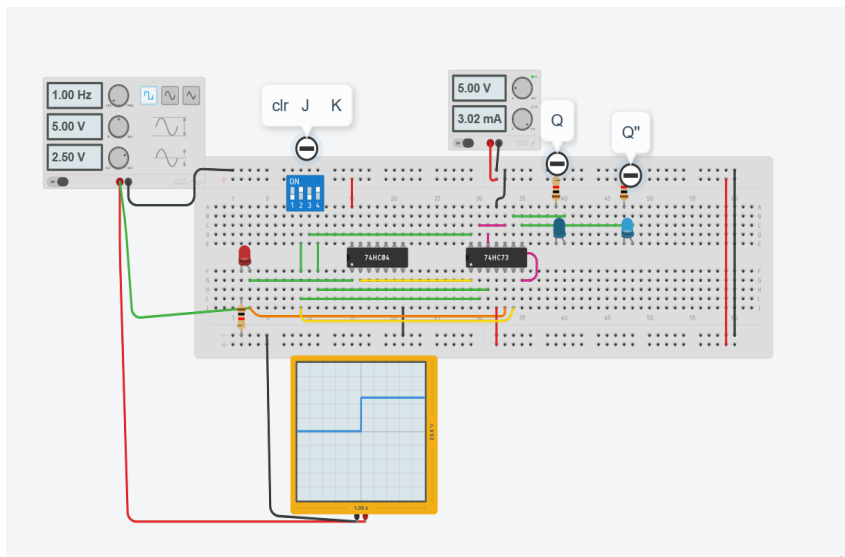

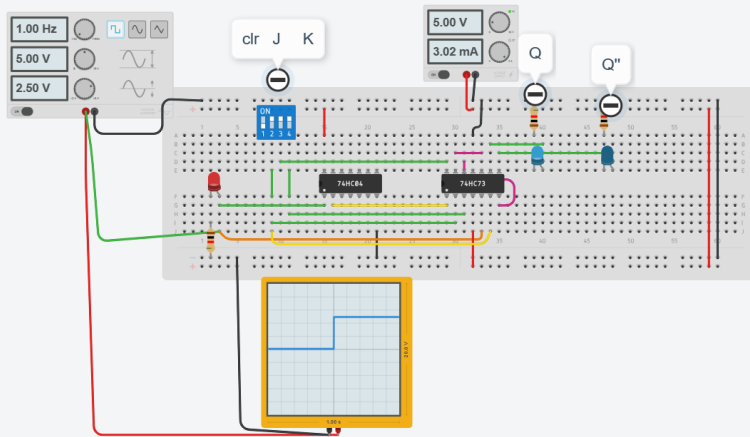

Here

CLK = 1

J = 1


K = 1

Q = Q'

Q' = Q

STATE =

TOGGLE(OPPOSITE SITE)

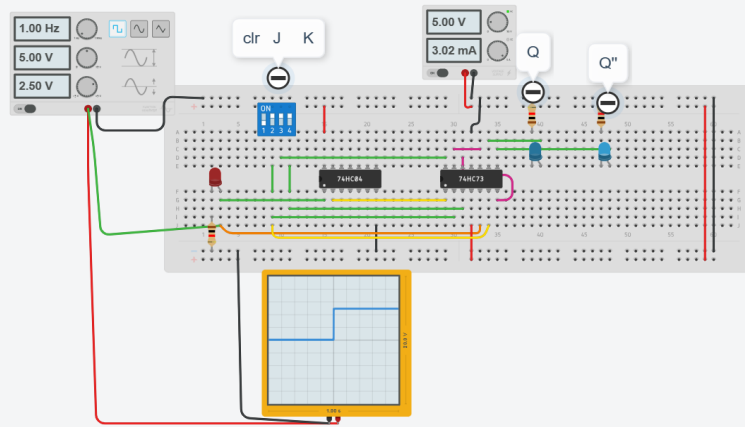

— END —